

REVISION STELR (Electric Circuits) 2013


- 1** The voltage across a load in an electric circuit is a measure of:
- A the amount of electric charge passing through the load in each second
 - B the amount of energy gained or lost by electric charge as it moves through the load
 - C the amount of electrical energy transformed in the load during each second
 - D the electric current travelling through the load.

-
- 2** The flow of electric charge in an electric circuit is called:
- A electric current
 - B electric power
 - C resistance
 - D voltage.

-
- 3** An ammeter is used to measure:
- A electrical energy
 - B resistance
 - C voltage
 - D electric current.
-

4 If the filament in light-globe K shown in the following circuit diagram breaks:

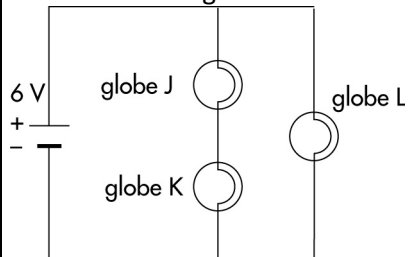- A globes J and L will both stop glowing
- B globes J and L will continue to glow
- C globe J will stop glowing and globe L will continue to glow
- D globe L will stop glowing and globe J will continue to glow.






5 The watt is a unit of:

- A electric current
- B energy
- C power
- D voltage.

6 The amount of electrical energy transformed by a 5000 W air conditioner during 10 hours of operation is:



- A 50 000 kWh
- B 50 kWh
- C 50 000 J
- D 5000 kJ
- E 180 kJ
- F 1 800 000 kJ.

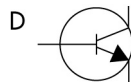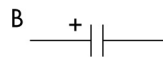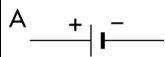7 Which of the following symbols represents a battery in an electric circuit diagram?



Short Answer:

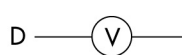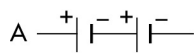
8 State which part of an electric circuit is represented by each of the following symbols.



9 What produces electric currents?


10 In a light bulb, what two forms of energy is electrical energy changed into?

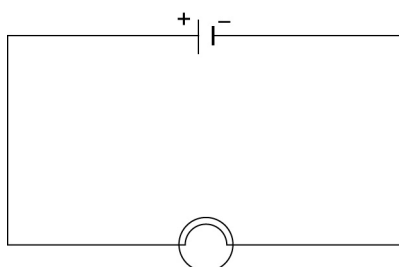- 11** Draw a circuit diagram to show where a voltmeter and ammeter should be placed in the following circuit to correctly measure the voltage across the globe and the current flowing through it. Use + and – signs on the meter symbols.




- 12** Explain why the conducting paths in electric appliances are usually made of metals like copper?

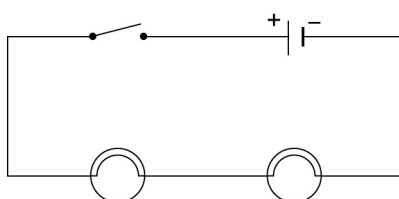- 13** Describe the circuit shown below in words.



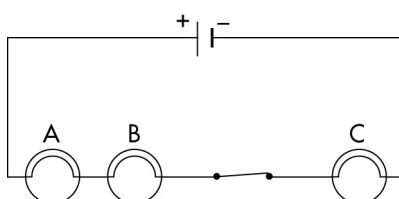- 14** In the electric circuit below, which lamps will stop glowing if the switch is opened?



- 15** Draw (a) a series and (b) a parallel circuit, with a 12 volt battery and three globes in each. Explain what would happen if one globe 'blew' in each circuit.

17	The lights in a house are connected in parallel with each other. State two advantages of connecting them in parallel rather than in series.
18	<p>The electric power delivered to an electronic device can be calculated using the formula</p> <p>$P = VI$ where P = power in watts, V = voltage and I = electric current in amperes.</p> <p>Imagine that you are required to measure the power delivered to a coil of wire in an electric kettle. Assume that the coil has been removed from the kettle. The coil of wire can be represented in a circuit diagram as a resistor.</p> <p>(a) List all of the equipment that you would need. (b) Use the appropriate symbols to draw a circuit diagram to represent the electric circuit used to perform the test.</p>


ANSWERS

1/ B 2/ A 3/ D 4/ C 5/ C 6/ B 7/ A

8/ A: battery or two cells in series B: open switch C: light globe D: voltmeter

9/ The flow of negatively charged electrons. 10/ Heat and light.


11/ 12/ Copper is a good conductor.

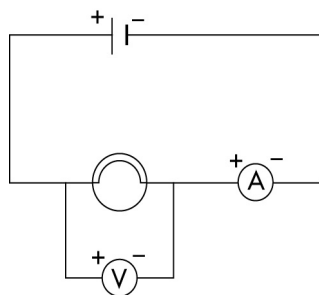


13/ Two light globes, a cell and a switch are all connected in series. The switch is open.

14/ All three of A, B and C.

15/ (a)

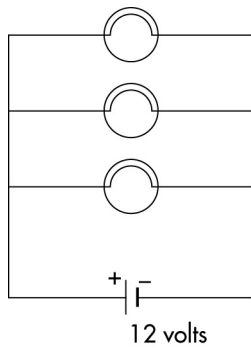

(b)

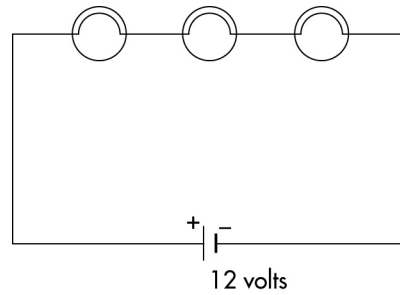

(a) If one bulb 'blows', the other two may get brighter. (b) If one bulb 'blows' all bulbs go out.

16/ (a) A, B (b) A, B, C (c) None

17/ Two of: If one light 'blows', the others are not affected at all. For lights in series, a 'blown' light could not be identified as easily because all lights would stop working. In a series circuit, adding more lights would cause the rest to be dimmer and you could not turn on individual lights; they would have to be all on or all off.

(a) 18/ (a) Power supply, connecting leads, ammeter, voltmeter

(b)

